

## Basic Electronic Devices and Circuits

### FET Solution

1.

$$(a) V_{GS_Q} = -\bar{V}_{GG} = -2 \text{ V}$$

$$(b) I_{D_Q} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left( 1 - \frac{-2 \text{ V}}{-8 \text{ V}} \right)^2 \\ = 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625) \\ = \mathbf{5.625 \text{ mA}}$$

$$(c) V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega) \\ = 16 \text{ V} - 11.25 \text{ V} = \mathbf{4.75 \text{ V}}$$

2.

(a) & (b)

$$I_{DQ} = I_{DSS} (1 - V_{GS}/V_P)^2 = 8(1 + V_{GS}/6)^2 \quad \text{--- (i)}$$

$$V_{GS} = -I_{DQ} \times R_S = -I_{DQ} \quad \text{----- (ii)}$$

From Equations (i) & (ii)

$$\mathbf{I_{DQ} = 2.59 \text{ mA and } V_{GS} = -2.59 \text{ V}}$$

$$\textcircled{C} \quad \mathbf{V_{DS} = 20 - 2.59(3.3+1) = 8.86 \text{ V}}$$

3. (a)  $I_{DQ} = I_{DSS} (1 - V_{GS}/V_P)^2 = 8(1 + V_{GS}/4)^2 \quad \text{--- (i)}$

$$V_{GS} = 1.82 - I_{DQ} \times R_S = 1.82 - 1.5 I_{DQ} \quad \text{----- (ii)}$$

From Equations (i) & (ii)

$$\mathbf{I_{DQ} = 2.414 \text{ mA and } V_{GS} = -1.8 \text{ V}}$$

$$\text{(b) } \mathbf{V_{DS} = 16 - 2.4(2.4+1.5) = 6.64 \text{ V}}$$

$$\textcircled{C} \quad \mathbf{V_{DG} = V_{DS} - V_{GS} = 8.44 \text{ V}}$$

4.

The level of  $V_G$  is determined as follows:

$$V_G = \frac{47 \text{ k}\Omega(16 \text{ V})}{47 \text{ k}\Omega + 91 \text{ k}\Omega} = 5.44 \text{ V}$$

with

$$\begin{aligned} I_D &= \frac{V_{DD} - V_D}{R_D} \\ &= \frac{16 \text{ V} - 12 \text{ V}}{1.8 \text{ k}\Omega} = 2.22 \text{ mA} \end{aligned}$$

The equation for  $V_{GS}$  is then written and the known values substituted:

$$\begin{aligned} V_{GS} &= V_G - I_D R_S \\ -2 \text{ V} &= 5.44 \text{ V} - (2.22 \text{ mA})R_S \\ -7.44 \text{ V} &= -(2.22 \text{ mA})R_S \end{aligned}$$

and

$$R_S = \frac{7.44 \text{ V}}{2.22 \text{ mA}} = 3.35 \text{ k}\Omega$$

The nearest standard commercial value is 3.3 k $\Omega$ .

5.

(a)

At  $V_{GS} = -0.5 \text{ V}$ ,

$$g_m = g_{m0} \left[ 1 - \frac{V_{GS}}{V_P} \right] = 4 \text{ mS} \left[ 1 - \frac{-0.5 \text{ V}}{-4 \text{ V}} \right] = 3.5 \text{ mS} \quad (\text{versus } 3.5 \text{ mS} \text{ graphically})$$

Part B: PNP Small-Signal Analysis

(b) & (C)

At  $V_{GS} = -1.5 \text{ V}$ ,

$$g_m = g_{m0} \left[ 1 - \frac{V_{GS}}{V_P} \right] = 4 \text{ mS} \left[ 1 - \frac{-1.5 \text{ V}}{-4 \text{ V}} \right] = 2.5 \text{ mS}$$

At  $V_{GS} = -2.5 \text{ V}$ ,

$$g_m = g_{m0} \left[ 1 - \frac{V_{GS}}{V_P} \right] = 4 \text{ mS} \left[ 1 - \frac{-2.5 \text{ V}}{-4 \text{ V}} \right] = 1.5 \text{ mS}$$

6.

### Solution

$$(a) \ g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(10 \text{ mA})}{8 \text{ V}} = 2.5 \text{ mS}$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GS_2}}{V_P} \right) = 2.5 \text{ mS} \left( 1 - \frac{(-2 \text{ V})}{(-8 \text{ V})} \right) = \mathbf{1.88 \text{ mS}}$$

$$(b) \ r_d = \frac{1}{y_{os}} = \frac{1}{40 \ \mu\text{S}} = \mathbf{25 \text{ k}\Omega}$$

$$(c) \ Z_i = R_G = \mathbf{1 \text{ M}\Omega}$$

$$(d) \ Z_o = R_D \| r_d = 2 \text{ k}\Omega \| 25 \text{ k}\Omega = \mathbf{1.85 \text{ k}\Omega}$$

$$(e) \ A_v = -g_m(R_D \| r_d) = -(1.88 \text{ mS})(1.85 \text{ k}\Omega) \\ = \mathbf{-3.48}$$

$$(f) \ A_v = -g_m R_D = -(1.88 \text{ mS})(2 \text{ k}\Omega) = \mathbf{-3.76}$$

As demonstrated in part (f), a ratio of  $25 \text{ k}\Omega : 2 \text{ k}\Omega = 12.5 : 1$  between  $r_d$  and  $R_D$  resulted in a difference of 8% in solution.

7.

$$(a) \quad g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(16 \text{ mA})}{4 \text{ V}} = 8 \text{ mS}$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GS_o}}{V_P} \right) = 8 \text{ mS} \left( 1 - \frac{(-2.86 \text{ V})}{(-4 \text{ V})} \right) = \mathbf{2.28 \text{ mS}}$$

$$(b) \quad r_d = \frac{1}{y_{os}} = \frac{1}{25 \mu\text{S}} = \mathbf{40 \text{ k}\Omega}$$

$$(c) \quad Z_i = R_G = \mathbf{1 \text{ M}\Omega}$$

(d) With  $r_d$ :

$$\begin{aligned} Z_o &= r_d \| R_S \| 1/g_m = 40 \text{ k}\Omega \| 2.2 \text{ k}\Omega \| 1/2.28 \text{ mS} \\ &= 40 \text{ k}\Omega \| 2.2 \text{ k}\Omega \| 438.6 \Omega \\ &= \mathbf{362.52 \Omega} \end{aligned}$$

revealing that  $Z_o$  is often relatively small and determined primarily by  $1/g_m$ . Without  $r_d$ :

$$Z_o = R_S \| 1/g_m = 2.2 \text{ k}\Omega \| 438.6 \Omega = \mathbf{365.69 \Omega}$$

revealing that  $r_d$  typically has little impact on  $Z_o$ .

(e) With  $r_d$ :

$$\begin{aligned} A_v &= \frac{g_m(r_d \| R_S)}{1 + g_m(r_d \| R_S)} = \frac{(2.28 \text{ mS})(40 \text{ k}\Omega \| 2.2 \text{ k}\Omega)}{1 + (2.28 \text{ mS})(40 \text{ k}\Omega \| 2.2 \text{ k}\Omega)} \\ &= \frac{(2.28 \text{ mS})(2.09 \text{ k}\Omega)}{1 + (2.28 \text{ mS})(2.09 \text{ k}\Omega)} = \frac{4.77}{1 + 4.77} = \mathbf{0.83} \end{aligned}$$

which is less than 1 as predicted above.

Without  $r_d$ :

$$\begin{aligned} A_v &= \frac{g_m R_S}{1 + g_m R_S} = \frac{(2.28 \text{ mS})(2.2 \text{ k}\Omega)}{1 + (2.28 \text{ mS})(2.2 \text{ k}\Omega)} \\ &= \frac{5.02}{1 + 5.02} = \mathbf{0.83} \end{aligned}$$

revealing that  $r_d$  usually has little impact on the gain of the configuration.

## 8. After converting the voltage divider network $R_1$ and $R_2$

To Thevenin Equivalent Circuit

$$R_{TH} = (10 \times 90) / (10 + 90) = 9 \text{ M}\Omega$$

$$V_{TH} = (18 \times 10) / (10 + 90) = 1.8 \text{ V}$$

Applying KVL in input loop with  $V_{TH}$  &  $R_{TH}$

$$1.8 = I_G R_{TH} + V_{GS} + I_D R_S \quad \text{----- (i)}$$

$$I_D = I_{DSS}(1 - V_{GS}/V_P)^2 = 8(1 - V_{GS}/4)^2 \quad \text{----- (ii)}$$

From Equation (i) & (ii)

$$V_{GS} = 0.1 \text{ V and } I_D = 7.6 \text{ mA}$$

$$g_{mo} = (2 I_{DSS} / |V_P|) = 0.004 \text{ A/V}$$

$$g_m = g_{mo} (I_{DQ} / I_{DSS})^{1/2} = 0.0039 \text{ A/V}$$

$$A_v = V_o/V_i = (-g_m R_D v_{gs})/v_{gs} \\ = -7.8$$

$$Z_i = V_i/I_i = R_G = R_{TH} = 9 \text{ M}\Omega$$

$$Z_o = V_o/I_o = (-g_m R_D v_{gs})/(-g_m v_{gs}) \\ = R_D = 2 \text{ K}\Omega$$